

Chapter 1: Electric Circuit Variables

ECE 2040

1 Definitions

Students who have taken Physics 2 are likely to know these already.

- **Electric Circuit/Network:** Interconnection of electrical elements linked together in a closed path so that an electric current may flow continuously.
- **Charge:** Quantity of electricity responsible for electric phenomena.
- **Current:** Time rate of flow of electric charge past a given point

$$i = \frac{dq}{dt}$$

- **Direct Current:** Current of constant magnitude
- **Voltage** across an element is the work required to move a unit positive charge from the -ve terminal to the +ve terminal.



$$v = \frac{dw}{dq}$$

- **Power:** Time rate of supplying or receiving power

$$p = \frac{dw}{dt}$$

2 Passive Convention

TABLE 1
PASSIVE SIGN CONVENTIONS

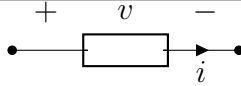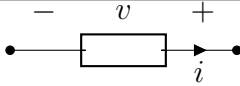Passive Convention	Non-Passive Convention
	
Power <i>received</i> by element	Power <i>supplied</i> by element