

Chapter 6: The Operational Amplifier

ECE 2040

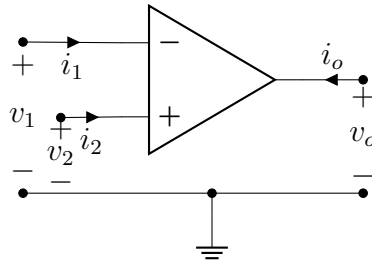


Figure 1. The Operational Amplifier, with inputs/outputs labeled.

- **Linear Op Amp:** Op-amps whose inputs/outputs satisfy the below three conditions:

$$|v_o| \leq v_{sat}$$

$$|i_o| \leq i_{sat}$$

$$\left| \frac{dv_o(t)}{dt} \right| \leq SR$$

where,

- v_{sat} = saturation voltage
- i_{sat} = saturation current
- SR = slew rate limit

- **Ideal Op Amp:** A linear operational amplifier that meets the following conditions:

1. $i_1 = 0$
2. $i_2 = 0$
3. $v_1 = v_2$

Note that v_1 and v_2 are not shorted. Also, i_o is not necessarily 0 V.

Applying NVA on an Op-Amp

- Using the property $v_1 = v_2$, eliminate one of the node voltage equations
- Exploit the property $i_1 = i_2 = 0$ by using KCL at the input nodes of the op amp.
- Since $i_o \neq 0$, do not apply KCL at this node - doing so will add an unknown.