

Chapter 7: Energy Storage Elements

ECE 2040



Figure 1. Energy Storage Elements in a circuit.

Capacitors

- **Capacitance:** Measure of ability of a device to store energy in the form of a separated charge or electric field.

$$q(t) = Cv(t)$$

where,

$\Rightarrow q(t)$ = charge stored by the capacitor

$\Rightarrow C$ = capacitance of the capacitor

$\Rightarrow v(t)$ = voltage across the capacitor

- Current across the capacitor can be found by integrating above equation.

$$i(t) = C \frac{dv(t)}{dt}$$

- Voltage across a capacitor w.r.t. current:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

where,

$\Rightarrow t_0$ = initial time (usually 0s, depends on question)

- Energy stored in a capacitor

$$w_c = \frac{1}{2} C v^2 \bigg|_{v(-\infty)}^{v(t)}$$

- A capacitor in a dc circuit behaves as an open circuit.

Series and Parallel Capacitors

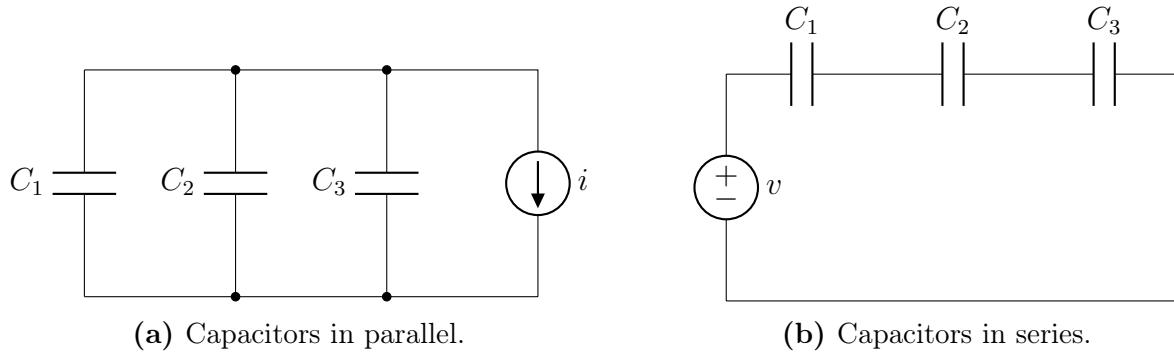


Figure 2. Combinations of capacitors.

- Capacitances in parallel add up:

$$C_p = C_1 + C_2 + C_3$$

- Inverses of capacitance in series add up:

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Inductors

- Inductance is a measure of the ability of a device to store energy in the form of a magnetic field.

$$v(t) = L \frac{di(t)}{dt}$$

- Current through an inductor

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

- Energy Stored in an inductor

$$w = \frac{1}{2} L i^2$$

- An inductor in a dc circuit behaves as a short circuit.

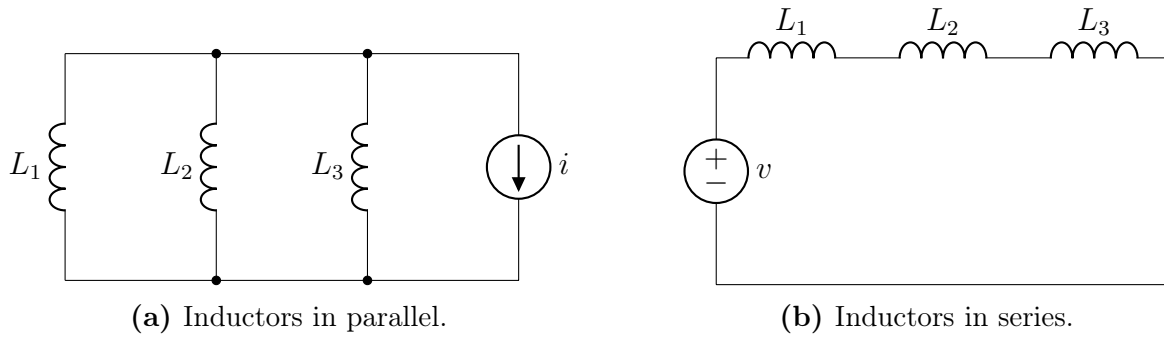


Figure 3. Combinations of inductors.

Series and Parallel Inductors

- Inductances in series add up:

$$L_s = L_1 + L_2 + L_3$$

- Inverses of inductances in parallel add up:

$$\frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$