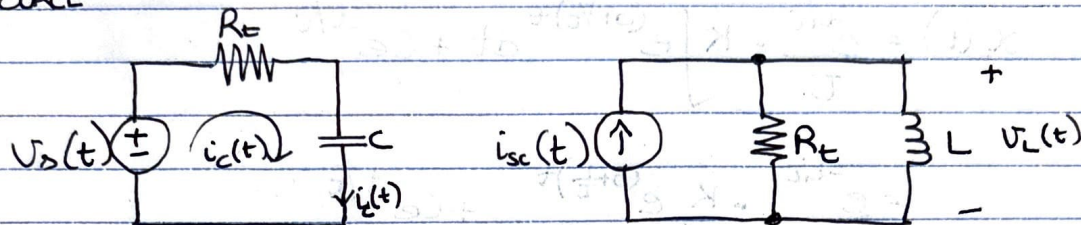


07/09/2025

DERIVATION OF RESPONSE OF A FIRST-ORDER CIRCUIT TO A NONCONSTANT SOURCE



$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$-V_s(t) + R_t \left(\frac{dV_c(t)}{dt} \right) + V_c(t) = 0$$

$$\frac{L}{R_t} \frac{di_L(t)}{dt} + i_L(t) = i_s(t)$$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R_t C} = \frac{+V_s(t)}{R_t C}$$

$(\tau = R_t C)$

$$\frac{di_L(t)}{dt} + \frac{i_L(t)}{L/R_t} = \frac{i_s(t)}{L/R_t}$$

$(\tau = L/R_t)$

Solve:

$$\mu(t) = e^{\int p(t) dt} = e^{\frac{1}{\tau} \int dt} = e^{t/\tau}$$

General form: $\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = \frac{s(t)}{\tau}$

$$\therefore x(t) \mu(t) = \frac{1}{\tau} \int \mu(t) s(t) dt + C \Rightarrow x(t) e^{t/\tau} = \frac{1}{\tau} \int s(t) e^{t/\tau} dt + C$$

$$\Rightarrow x(t) = \frac{e^{-t/\tau}}{\tau} \int s(t) e^{t/\tau} dt + C e^{-t/\tau}$$

I) If $s(t)$ is a constant (M):

$$x(t) = \frac{e^{-t/\tau}}{\tau} M \cdot \tau e^{t/\tau} + C e^{-t/\tau}$$

$$= M + C e^{-t/\tau} \equiv x_f + x_n, \quad x_f = M, \quad x_n = C e^{-t/\tau}$$

τ always remains $C e^{-t/\tau}$

When $x_f = K e^{bt}$: When $s(t) = K e^{bt}$

$$x(t) = \frac{e^{-t/\tau}}{\tau} \cdot K \int e^{(b+1/\tau)t} dt + C e^{-t/\tau}$$

$$= \underbrace{\frac{e^{-t/\tau}}{\tau}}_{x_f} \cdot K \underbrace{\frac{e^{(b+1/\tau)t}}{(b+1/\tau)}}_{x_n} + \underbrace{C e^{-t/\tau}}_{x_n}$$

Similarly, can generalize with lot more functions.