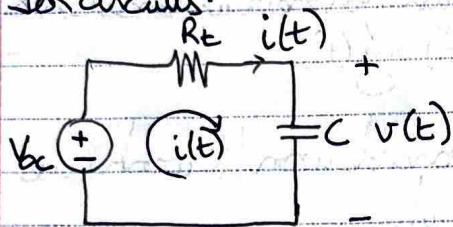


DERIVATION OF RESPONSE OF FIRST ORDER CIRCUIT TO A CONSTANT INPUT
For circuits:




$$i(t) = C \frac{dv(t)}{dt}$$

KCL:

$$-V_{oc} + i(t)R_t + v(t) = 0 \Rightarrow C \frac{dv(t)}{dt} R_t + v(t) = V_{oc}$$

$$\Rightarrow \frac{dv(t)}{dt} + \frac{v(t)}{R_t C} = \frac{V_{oc}}{R_t C}$$

————— (1)

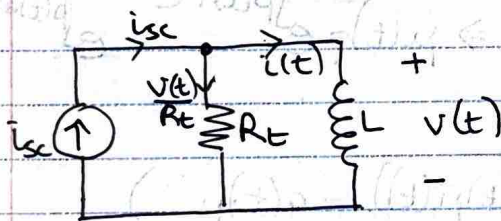

$$v(t) = L \frac{di(t)}{dt}$$

$$i_{sc} = \frac{v(t)}{R_t} + i(t) \Rightarrow \frac{L}{R_t} \frac{di(t)}{dt} + i(t) = i_{sc}$$

$$\Rightarrow \frac{di(t)}{dt} + \frac{i(t)}{\frac{L}{R_t}} = \frac{i_{sc}}{\frac{L}{R_t}}$$

————— (2)

Since (1) & (2) are similar, set 2 constants, τ and K

Set the new DE be: $\frac{dx(t)}{dt} + \frac{x(t)}{\tau} = K$

We can solve this DE: $\mu(t) = e^{\int \frac{1}{\tau} dt} = e^{\frac{t}{\tau}}$

$$\therefore x(t)e^{\frac{t}{\tau}} = \int K e^{\frac{t}{\tau}} + C$$

For (1):

$$\tau = R_t C, K = \frac{V_{oc}}{R_t C}$$

For (2):

$$\tau = \frac{L}{R_t}, K = \frac{i_{sc}}{\frac{L}{R_t}}$$

⊗ Assume K is constant:

$$\therefore x(t)e^{t/\tau} = K\tau e^{t/\tau} + C$$

$$\Rightarrow x(t) = K\tau + Ce^{-t/\tau}$$

$$\text{At } x=0, \quad x(0) = K\tau + C \quad \Rightarrow C = x(0) - K\tau$$

N.B $K\tau = V_{oc}$ for ①, I_{sc} for ② (let's say x_{TH} for this)

$$\therefore x(t) = x_{TH} + (x(0) - x_{TH})e^{-t/\tau}$$

$$\text{For ①: } V(t) = V_{oc} + (V(0) - V_{oc})e^{-t/Rc}$$

$$i(t) = I_{sc} + (i(0) - I_{sc})e^{-Rt/L}$$

— x —