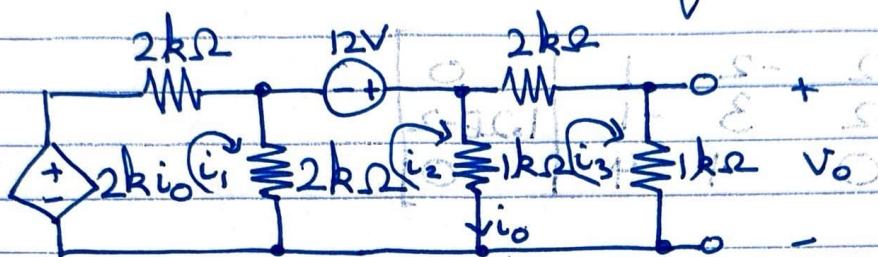


Summer 2020, Exam 1, Problem 2 (find V_o)



$2k = 2 \times 10^3$
SI units!

Use Mesh Current Analysis:

$$i_o = (i_2 - i_3)$$

$$M1: -2k i_o + 2k i_1 + 2k (i_1 - i_2) = 0$$

$$\text{sub ①: } -2E3(i_2 - i_3) + 2E3 i_1 + 2E3(i_1 - i_2) = 0$$

$$\Rightarrow (2E3 + 2E3)i_1 - (2E3 + 2E3)i_2 + 2E3 i_3 = 0$$

$$\Rightarrow 4E3 i_1 - 4E3 i_2 + 2E3 i_3 = 0$$

$$\Rightarrow 2i_1 - 2i_2 + i_3 = 0$$

$$\text{sub M2: } 2E3(i_2 - i_1) - 12 + 1E3(i_2 - i_3) = 0$$

$$\Rightarrow -2E3 i_1 + 3E3 i_2 - 1E3 i_3 = 12$$

$$\Rightarrow -2i_1 + 3i_2 - i_3 = 12E-3$$

$$M3: 1E3(i_3 - i_2) + 2E3(i_3) + 1E3(i_3) = 0$$

$$\Rightarrow -1E3 i_2 + (2E3 + 1E3 + 1E3)i_3 = 0$$


$$\Rightarrow -i_2 + 4i_3 = 0$$

Put ②, ③, ④ in a matrix:

$$\begin{bmatrix} 2 & -2 & 1 & | & 0 \\ -2 & 3 & -1 & | & 1.2E-2 \\ 0 & -1 & 4 & | & 0 \end{bmatrix}$$

Solve: $i_1 = 0.0105A$, $i_2 = 0.012A$, $i_3 = 0.003A$

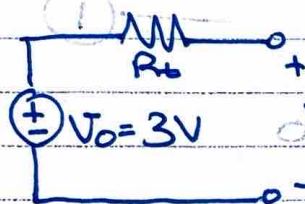
$$\therefore V_o = i_3 (1k\Omega) = 3E-3 A \times 1E3V = \boxed{3V}$$



There is no need to calculate R_o here.
The solution key treats $1k\Omega$ resistor as load and solves the rest using Thévenin's theorem.

⊗ If in doubt, ask the professor regarding which circuit element should be taken as load, if any.

This is what solution did:

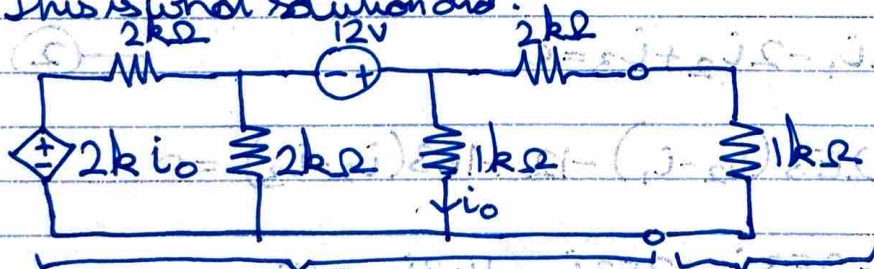

source (solved using Thévenin) load

$$0 = (i_1) 2k\Omega + (i_2) 2k\Omega + (i_3) 1k\Omega$$

$$0 = 2k(i_1 + i_2 + i_3) + 1k i_3$$

(P)---

$$0 = 2k i_1 + 2k i_2 + 3k i_3$$