
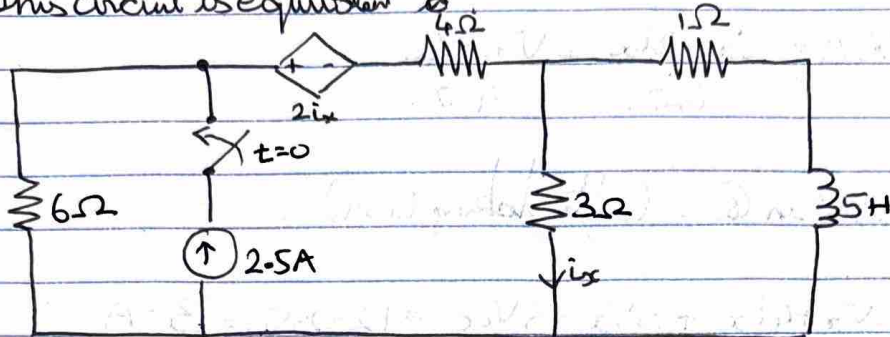


8.6-13

This circuit is equivalent to:

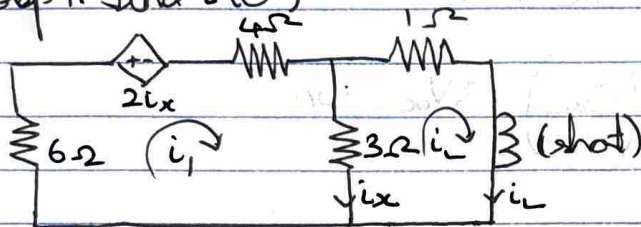

Step 1: Find $i(0^+)$



Use MCA
 $i_x = i_1 - i_L$

$$10i_1 + 2i_x + 3(i_1 - i_L) = 0 \Rightarrow 10i_1 + 5(i_1 - i_L) = 0$$

$$\Rightarrow 15i_1 - 5i_L = 0 \Rightarrow 3i_1 - i_L = 0 \quad \text{--- (1)}$$


Mesh 2: $3(i_L - i_1) + 1i_L = 0$

$$\Rightarrow 4i_L - 3i_1 = 0 \Rightarrow 3i_1 - 4i_L = 0 \quad \text{--- (2)}$$

add (1) & (2): $4i_L - i_L = 0 \Rightarrow i_L = 0$

$$\therefore i(0^+) = i(0^-) = 0A \quad \text{--- (3)}$$

Step 2: Find Norton equivalent

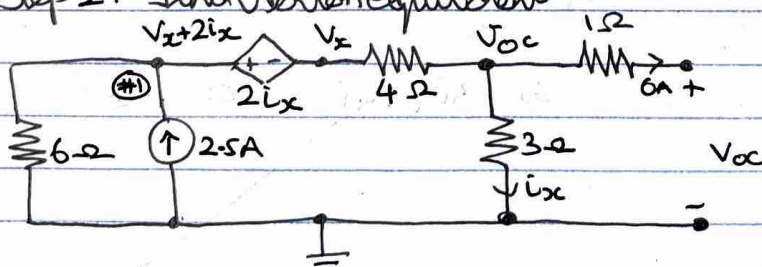

$$i_x = \frac{V_{oc}}{3} \quad \text{--- (4)}$$

$$\frac{V_x - V_{oc}}{4} = \frac{V_{oc}}{3} \Rightarrow 3V_x - 3V_{oc} = 4V_{oc} \Rightarrow V_x = \frac{7V_{oc}}{3} \quad \text{--- (5)}$$

Apply KCL at #1:

$$2.5A = \frac{V_x + 2i_x}{6\Omega} + \frac{V_x - V_{oc}}{4\Omega}$$

— (6)

Subs (4), (5) in (6): (after taking LCM)

$\frac{2 \times 4, 6}{2, 3}$

$$2V_x + 4i_x + 3V_x - 3V_{oc} = 12 \times 2.5A = 30A$$



$$\Rightarrow 5V_x + 4i_x - 3V_{oc} = 30A$$

$$\Rightarrow 5\left(\frac{7V_{oc}}{3}\right) + 4\left(\frac{V_{oc}}{3}\right) - 3V_{oc} = 30A$$

$$\Rightarrow 35V_{oc} + 4V_{oc} - 9V_{oc} = 90A$$

$$\Rightarrow 30V_{oc} = 90A \Rightarrow V_{oc} = 3V$$

— (7)

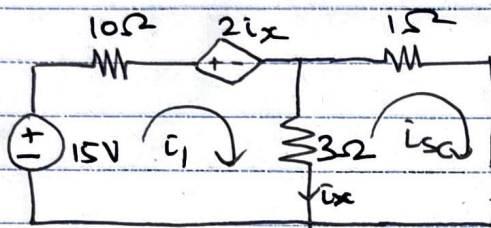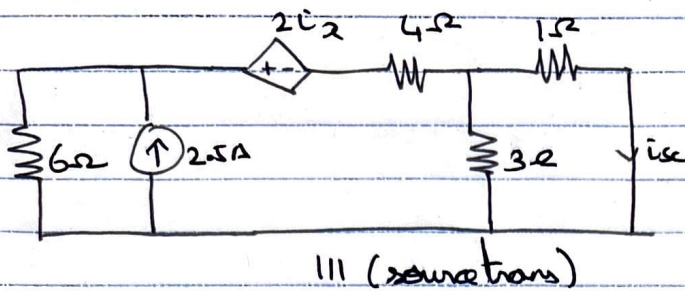

$$i_x = i_1 - i_{sc} \quad \text{--- (8)}$$

$$3i_x + 10i_1 + 2i_x = 15V \quad \text{--- (8)} \Rightarrow 10i_1 + 5(i_1 - i_{sc}) = 15V$$


$$\Rightarrow 15i_1 - 5i_{sc} = 15V \quad \text{--- (9)} \Rightarrow 5i_1 - i_{sc} = 5V$$

$$3(i_{sc} - i_1) + 1i_{sc} = 0 \Rightarrow -3i_1 + 4i_{sc} = 0 \quad \text{--- (10)}$$

$$\text{--- (9)} + 5 \times \text{--- (10)} = -5i_{sc} + 20i_{sc} = 15V$$

$$\therefore i_{sc} = \frac{15}{15} = 1A$$
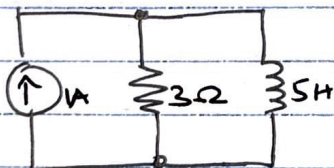
$$\therefore R_T = \frac{V_{oc}}{I_{sc}} = 3\Omega \quad \text{--- (11)}$$



$$\therefore i(t) = I_{sc} + (i(0^+) - I_{sc}) e^{-t/(R_T/L)}$$

③, ⑪

$$i(t) = 1 + (0 - 1) e^{-t/(3/5)}$$

$$\therefore i(t) = 1 - e^{-t(3/5)} \quad t \geq 0$$